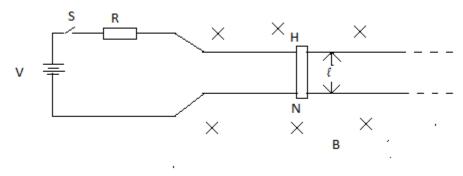
1. In the diagram, the circuit is set on a rigid frame, and HN bar is a conductor with mass m and it can move along the frictionless track which can be considered infinitely long. Separation between the two parallel wires of the track is I. A uniform magnetic field B, vertically downward on the page, has been set throughout the entire system.



- a. When the switch is closed HN bar will start to move along the track. In which direction will the bar move?
- b. Find an expression for the velocity u of the bar using the given terms. What will be the highest magnitude of that velocity?
- c. Now the DC voltage source is replaced by a pulsating source with rectangular wave form of frequency .2 Hz. It gives +20V in first 5 seconds, and -20V in next 5 seconds; this way its polarity flips after every 5 seconds. It is given that

R = 10 ohm

L = 1m

M = .25kg

B = .5T


If the switch is closed at t = 0s, determine the velocity of the bar at t = 10s.

2. For a single slit diffraction experiment monochromatic light of wavelength λ is used. Find an expression for the intensity at a point P, whose angular separation from central maximum is θ . Slit width is d and the intensity of the central maximum is I_0 .

4


3. Through a leak of a kerosene ($\mu=1.2$) tank oil has fallen into see and has created a slick on top of the water ($\mu=1.33$). If someone looks straight down form a helicopter onto a region of the slick where the thickness is 465 nm, for which wavelengths of visible light is the reflection the greatest?

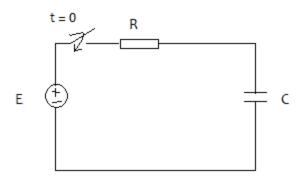4. It is given that when t = 0s, $q_o = 0$.



Find an expression for the charge q that accumulates on the positive plate of the capacitor at time t. 2

5.

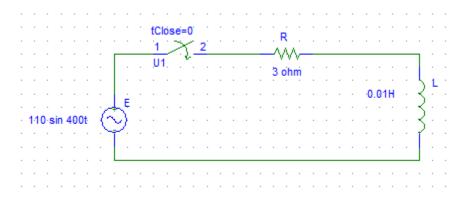

For above circuit-

a. Find total impedance.

1

3

- b. Find an expression for current i as a function of time t after closing the switch at t = 0s.
- c. Between voltage and current which one leads? Determine the phase shift of current.